

## Computer Project # 2


### *RLC-Circuits*

**Goal:** Investigate the charge on a capacitor in an  $RLC$  circuit with varying voltage.

**Tools needed:** `ode45`, `plot`.

**Description:** If  $Q(t)$  = charge on a capacitor at time  $t$  in an  $RLC$  circuit (with  $R, L$  and  $C$  being the resistance, inductance and capacitance, respectively, and  $E(t)$  = applied voltage), then Kirchoff's Laws give the following  $2^{nd}$  order differential equation for  $Q(t)$  :
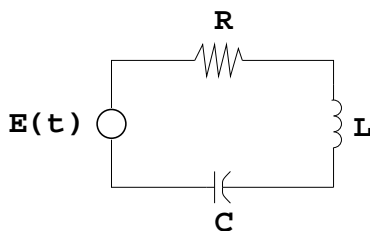
$$(*) \quad LQ''(t) + RQ'(t) + \frac{1}{C}Q(t) = E(t)$$



**Questions:** Assume  $L = 1$ ,  $C = \frac{1}{5}$ ,  $R = 4$  and  $E(t) = 10 \cos \omega t$ .

- (1) Use `ode45` (and `plot` routines) to plot the solution of (\*) with  $Q(0) = 0$  and  $Q'(0) = 0$  over the interval  $0 \leq t \leq 80$  for  $\omega = 0, 0.5, 1, 2, 4, 8, 16$ .
- (2) Let  $A(\omega) = \text{maximum of } |Q(t)| \text{ over the interval } 30 \leq t \leq 80$  (this approximates the amplitude of the steady-state solution). Experiment with various values of  $\omega$  and discuss what appears to happen to  $A(\omega)$  as  $\omega \rightarrow \infty$  and as  $\omega \rightarrow 0$ . Also, interpret your findings in terms of an equivalent spring-mass system.

**Remark:** There is an analogy between spring-mass systems and  $RLC$  circuits given by :

SPRING-MASS SYSTEM	$RLC$ CIRCUIT
$mu'' + cu' + ku = F(t)$	$LQ'' + RQ' + \frac{1}{C}Q = E(t)$
$u$ = Displacement	$Q$ = Charge
$u'$ = Velocity	$Q' = I$ = Current
$m$ = Mass	$L$ = Inductance
$c$ = Damping constant	$R$ = Resistance
$k$ = Spring constant	$1/C = (\text{Capacitance})^{-1}$
$F(t)$ = External force	$E(t)$ = Voltage