

## Computer Project # 2


### *RLC-Circuits*

**Goal:** Investigate the charge on a capacitor in an  $RLC$  circuit with varying voltage.

**Tools needed:** ode45, plot routines.

**Description:** If  $Q(t)$  = charge on a capacitor at time  $t$  in an  $RLC$  circuit (with  $R, L$  and  $C$  being the resistance, inductance and capacitance, respectively, and  $E(t)$  = applied voltage), then Kirchoff's Laws give the following 2<sup>nd</sup> order differential equation for  $Q(t)$  :
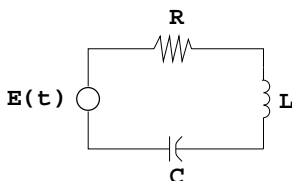
$$(*) \quad LQ''(t) + RQ'(t) + \frac{1}{C}Q(t) = E(t)$$



**Questions:** Assume  $L = 1$ ,  $C = \frac{1}{5}$ ,  $R = 4$  and  $E(t) = 8 \cos \omega t$ .

- (1) Use **ode45** (and plot routines) to plot the solution of (\*) with  $Q(0) = 0$  and  $Q'(0) = 0$  over the interval  $0 \leq t \leq 50$  for  $\omega = 0, 1, 2, 4, 8, 16$ .
- (2) For each of these 6 plots, find the largest value of  $|Q(t)|$  over  $30 \leq t \leq 50$  and fill in the table:

| $\omega$ | Max value of $ Q(t) $ on $30 \leq t \leq 50$ |
|----------|--|
| 0        |  |
| 1        |  |
| 2        |  |
| 4        |  |
| 8        |  |
| 16       |  |

- (3) Does increasing  $\omega$  appear to increase the maximum charge  $|Q(t)|$  on the capacitor? Interpret this result in terms of an equivalent spring-mass system.

**Remark:** There is an analogy between spring-mass systems and  $RLC$  circuits given by :

| SPRING-MASS SYSTEM       | RLC CIRCUIT                         |
|--------------------------|-------------------------------------|
| $mu'' + cu' + ku = F(t)$ | $LQ'' + RQ' + \frac{1}{C}Q = E(t)$  |
| $u$ = Displacement       | $Q$ = Charge                        |
| $u'$ = Velocity          | $Q' = I$ = Current                  |
| $m$ = Mass               | $L$ = Inductance                    |
| $c$ = Damping constant   | $R$ = Resistance                    |
| $k$ = Spring constant    | $1/C$ = (Capacitance) <sup>-1</sup> |
| $F(t)$ = External force  | $E(t)$ = Voltage                    |