

Meeting 6.2: Reversible computing and quantum circuits

I. RSAT

II. Quantum circuits


Next time: Solovay-Kitaev?

I. RSAT

Last time: a (Boolean) gate set \mathcal{G} is a set of bijections

$$\{0, 1\}^k \rightarrow \{0, 1\}^k \quad (k \text{ variable})$$

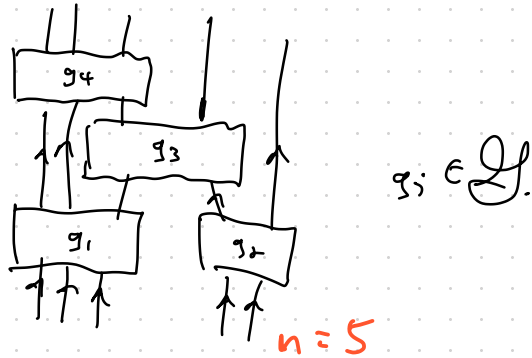A planar, reversible Boolean circuit R is a diagram like this:



R encodes a function

$$R: \{0, 1\}^n \rightarrow \{0, 1\}^n$$

The circuit is a "planar \mathcal{G} -factorization" of this function.

Note: every Boolean function (not necessarily reversible)


$$f: \{0,1\}^m \rightarrow \{0,1\}^n$$



can be built out of AND, OR, and NOT, FANOUT

{AND, OR, NOT} is a universal set of logic gates.

 If we want to find interesting computational problems for reversible circuits, \otimes better to "sufficiently rich."



Lots of wiggle room!

Example:

$\mathcal{U} = \{F\}$, where F is the Fredkin gate:

Inputs			Outputs		
a	b	c	a'	b'	c'
0	0	0	0	0	0
0	0	1	0	0	1
0	1	0	0	1	0
0	1	1	1	0	1
1	0	0	1	0	0
1	0	1	0	1	1
1	1	0	1	1	0
1	1	1	1	1	1

 



Figure 3.15. Fredkin gate truth table and circuit representation. The bits a and b are swapped if the control bit c is set, and otherwise are left alone.

Fredkin = "Controlled SWAP"

Given any $g: \{0,1\}^k \rightarrow \{0,1\}^k$

can always build "C-g" or "Controlled-g".

Just for fun: since F is "conservative"

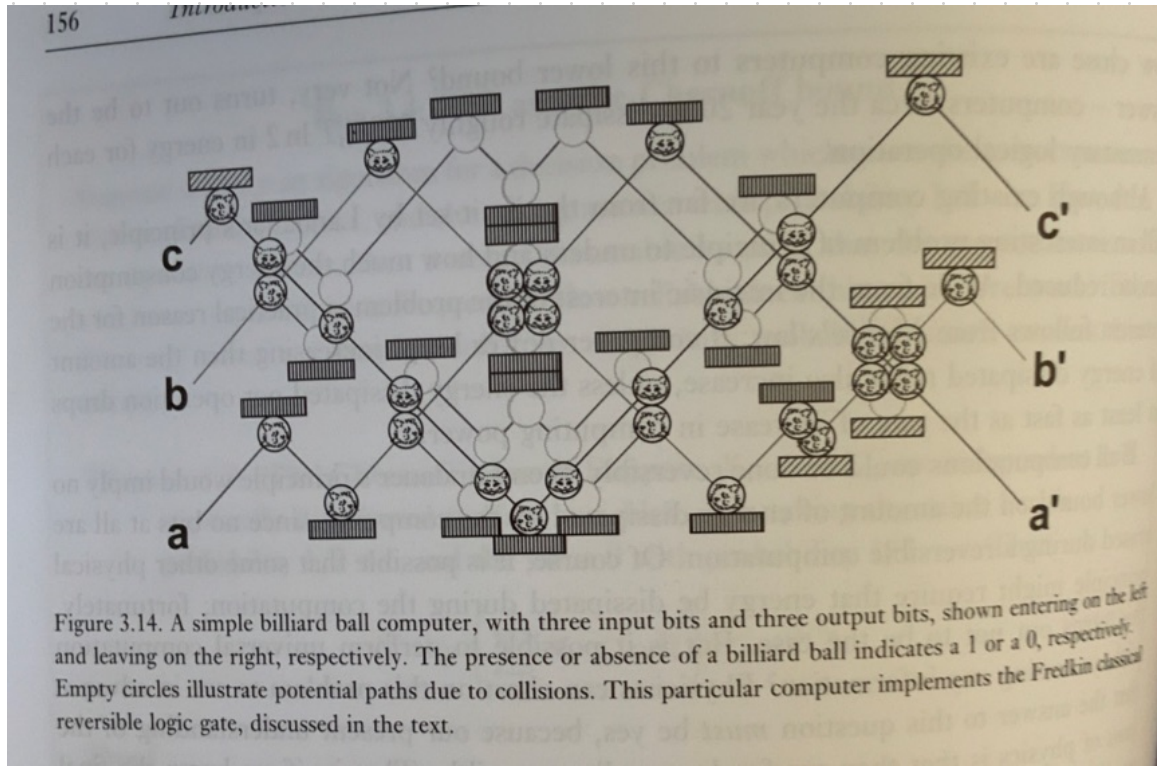

we can implement it with billiard balls!

If we allow extra "ancilla" bits, can encode AND, OR, NOT:


 


Figure 3.16. Fredkin gate configured to perform the elementary gates AND (left), NOT (middle), and a primitive routing function, the CROSSOVER (right). The middle gate also serves to perform the FANOUT operation, since it produces two copies of x at the output. Note that each of these configurations requires the use of extra 'ancilla' bits prepared in standard states – for example, the 0 input on the first line of the AND gate – and in general the output contains 'garbage' not needed for the remainder of the computation.

AN CILLA

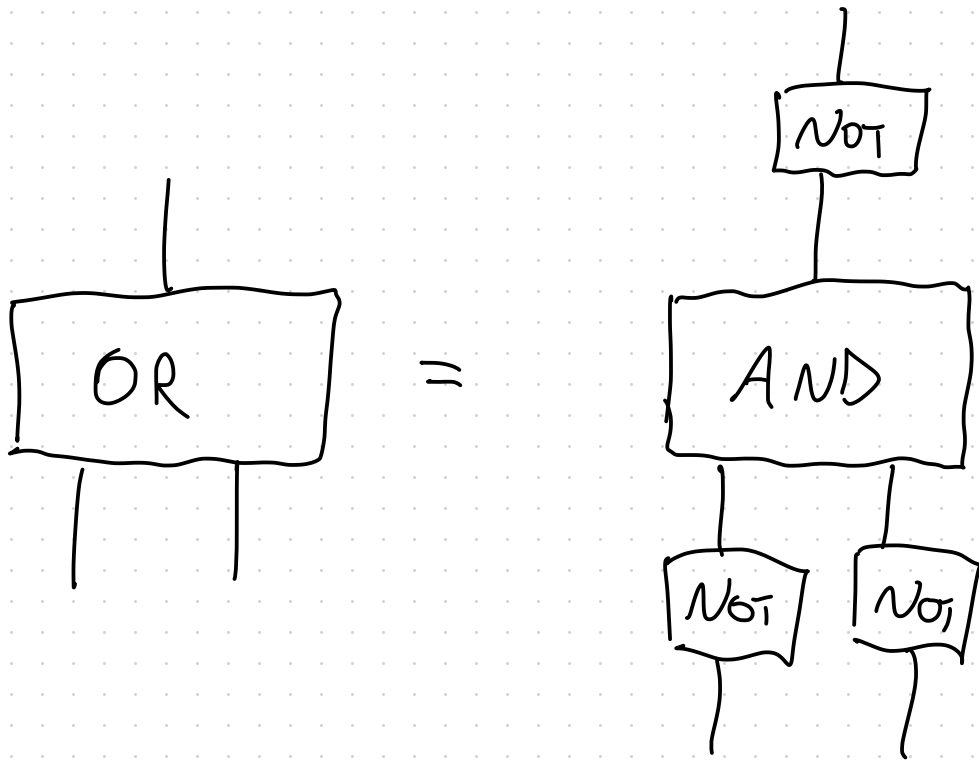Recall: De Morgan $x \vee y = \neg(\neg x \wedge \neg y)$



Since NOT and SWAP are reversible, might
as well include them in \mathcal{L} for now


$$\mathcal{L} = \{F, \text{NOT}, \text{SWAP}\}$$

$$\mathbb{C}^2 \longrightarrow \mathbb{C}^2 \otimes \mathbb{C}^2$$


$$X \longmapsto X \otimes X$$

is not linear!

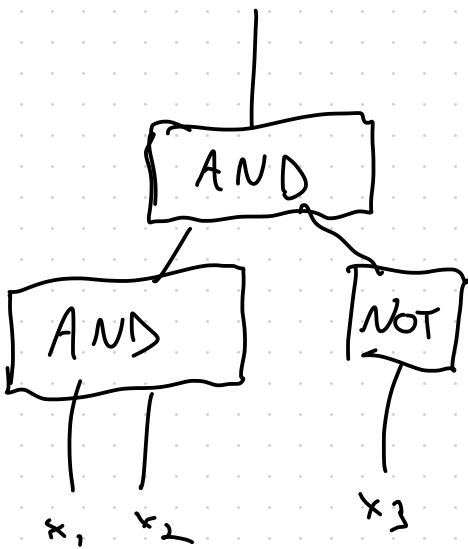We can "dilute" every Boolean circuit to a reversible circuit, by replacing every AND with a Fredkin + ancilla in 0 state:



dilate

 

$RSAT(\mathcal{G})$, variant 1:

$\mathcal{G} = \{F, SWAP, NOT\}$

Instance: reversible (planar) \mathcal{G} -circuit R , with input divided into "data register" of width d and "ancilla register" of width $n-d$, where $width(R) = n$, and all ancillae set to 0.


Problem: Does there exist $x \in \{0,1\}^d$ such that the first output bit of $R(x, \underbrace{0, \dots, 0}_{n-d})$ is 1?

Lemma: $RSAT(\mathcal{G})$ is NP-complete.

Proof: Reduce from CSAT using dilation as on previous page. \square

If we include COPY in \mathcal{L} , we can build a somewhat less contrived variant of RSAT.

Here COPY is

 

COPY is "reversible copy"
not "clone" or
"fan out"



(if $x=0$, COPY copies y to x .)

$$\mathcal{L} = \{ F, \text{SWAP}, \text{NOT}, \text{COPY} \}$$

RSAT (\mathcal{G}), variant 2:

Instance: \mathcal{G} -circuit R with $\text{width}(R) = 2n$, with input divided into data and ancilla registers both of width n .


Problem: Do there exist $x, y \in \{0, 1\}^n$ such that

$$R(x, \underbrace{0, \dots, 0}_{\text{ancilla}}) = (y, \underbrace{0, \dots, 0}_{\text{ancilla}})$$


Lemma: This problem is NP-complete.

Proof: Key idea is "uncomputation," which is also useful in quantum computation and in complexity results in topology. (See "Computational complexity and Σ -manifolds and zombies" by Kuperberg - S.)

Reduce from first variant. Three cases

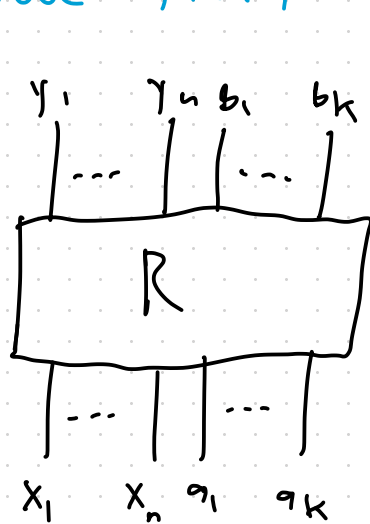


uncompute
 \rightarrow
 and apply
 a NOT

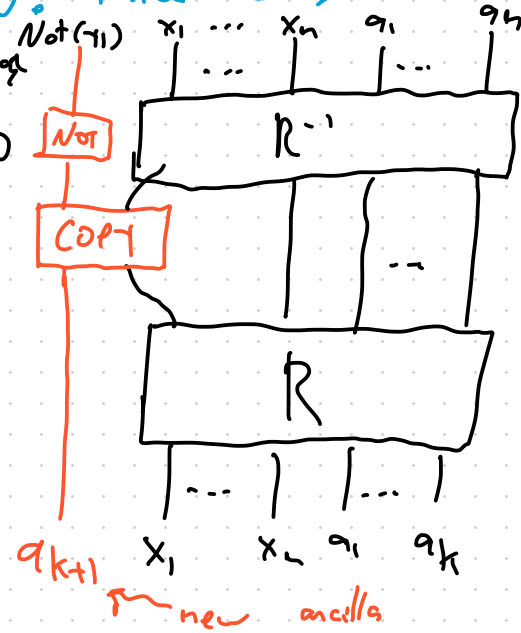


Case 5: $n = k + 1$

Case ii: $n > k+1$

 


uncompute
 and pad
 w/ new
 ancillae

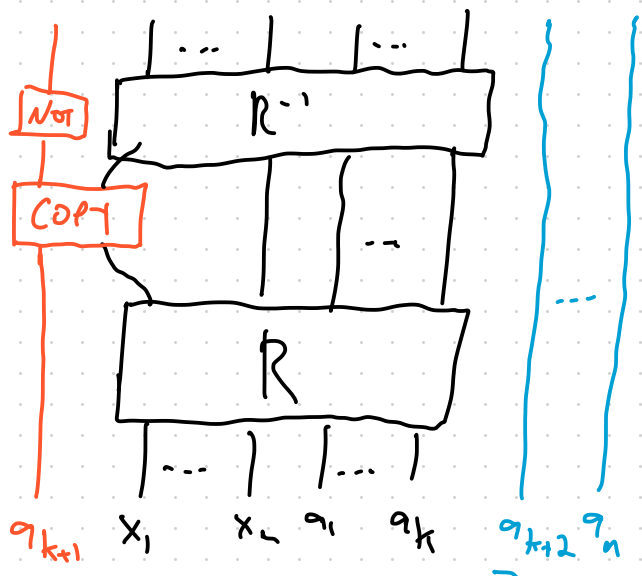


"padding
 ancilla register"

Case iii: $n < k+1$

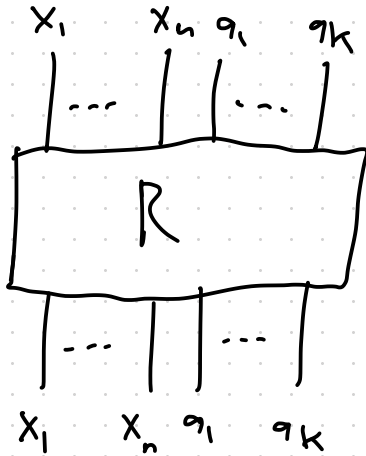

uncompute
and pad

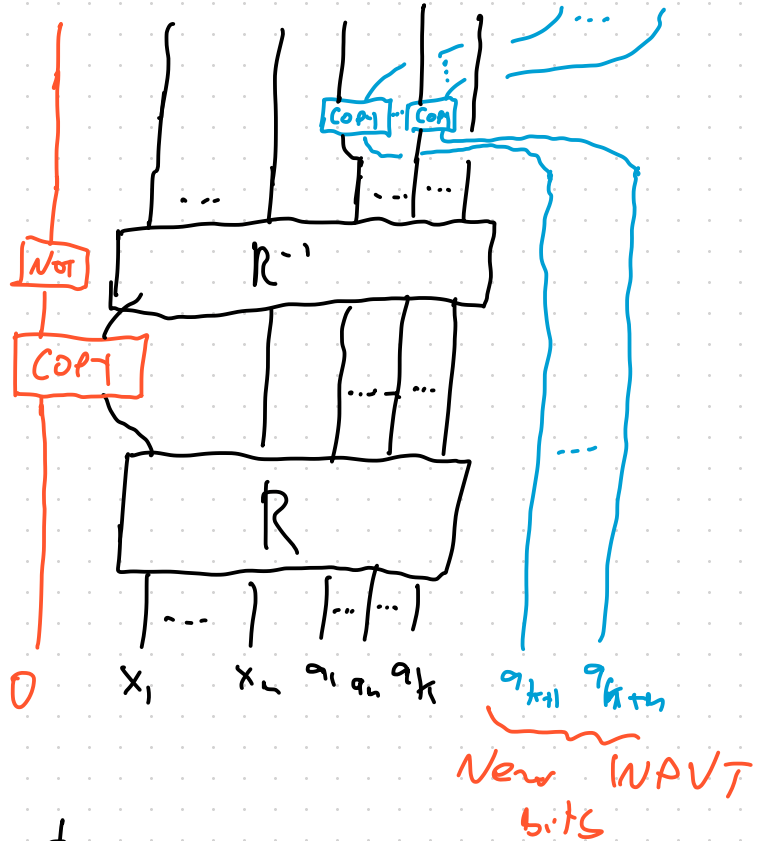


The copying at the end is to ensure a parsimonious reduction.



Why uncomputation is relevant to quantum computing:

We might work hard to prepare quantum state $|\psi\rangle$
so we can do useful things with it.

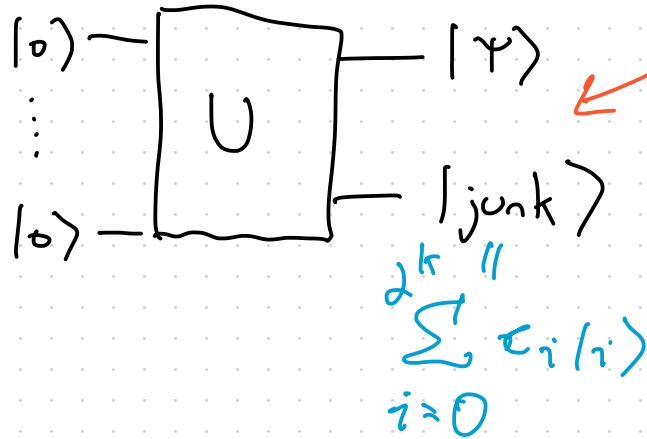

Potentially
imprecise notation!
Output might be
entangled w/ the
junk!

Interesting question:

Given gate set \mathcal{G} , what's the complexity of $\text{RSAT}(\mathcal{G})$?

ie.: "How powerful is \mathcal{G} ?"

Guess: Either its in P

or its NP-complete?

(See Schaefer dichotomy theorem.)

II. Quantum Circuits

Call a unitary transformation

$$U: \underbrace{\mathbb{C}^2 \otimes \dots \otimes \mathbb{C}^2}_k \rightarrow \mathbb{C}^2 \otimes \dots \otimes \mathbb{C}^2$$

a k -ary quantum gate.


Any set \mathcal{G} of quantum gates is called a ^{quantum} gate set.

Examples:

1. Any classical reversible gate g can be "linearized"

$$\begin{aligned} \text{If } g: \{0,1\}^k &\rightarrow \{0,1\}^k \\ (x_1, \dots, x_k) &\mapsto (y_1, \dots, y_k) \end{aligned}$$

Then

 

The quantum gate g permutes the computational basis of $(\mathbb{C}^2)^{\otimes k}$.

Take-away: quantum circuits include classical reversible circuits.

2. CNOT (aka COPY)

Linearization of CNOT



$$\text{CNOT} : \{0,1\}^2 \rightarrow \{0,1\}^2$$

$$00 \rightarrow 00$$

$$01 \rightarrow 01$$

$$10 \rightarrow 11$$

$$11 \rightarrow 10$$

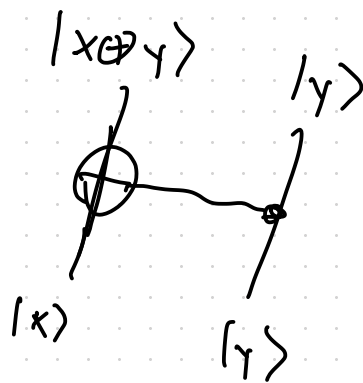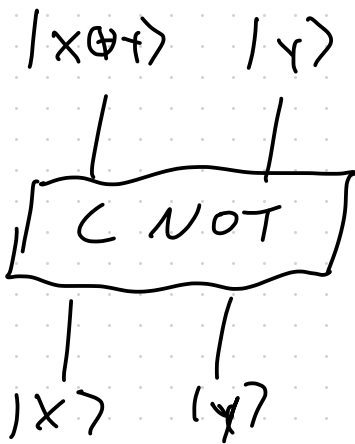

3. Single qubit gates i.e. unitary operators on \mathbb{C}^2 i.e.

Hadamard

$$H = \frac{1}{\sqrt{2}} \begin{pmatrix} 1 & 1 \\ 1 & -1 \end{pmatrix}$$

Lie group $U(d)$.

Phase gates:

$$\begin{array}{c} \uparrow \\ \boxed{e^{i\varphi}} \\ \uparrow \\ |x\rangle \end{array} = \begin{pmatrix} 1 & 0 \\ 0 & e^{i\varphi} \end{pmatrix} |x\rangle$$

$$a|0\rangle + b|1\rangle \mapsto a|0\rangle + e^{i\varphi} b|1\rangle.$$


A quantum circuit over \mathcal{G} is a circuit whose gates are elements of \mathcal{G} .

Just as for classical reversible circuits, quantum circuits have a width and a depth.

E.g.

C implements a unitary on $\mathbb{C}^2 \otimes \mathbb{C}^2 \otimes \mathbb{C}^2$:
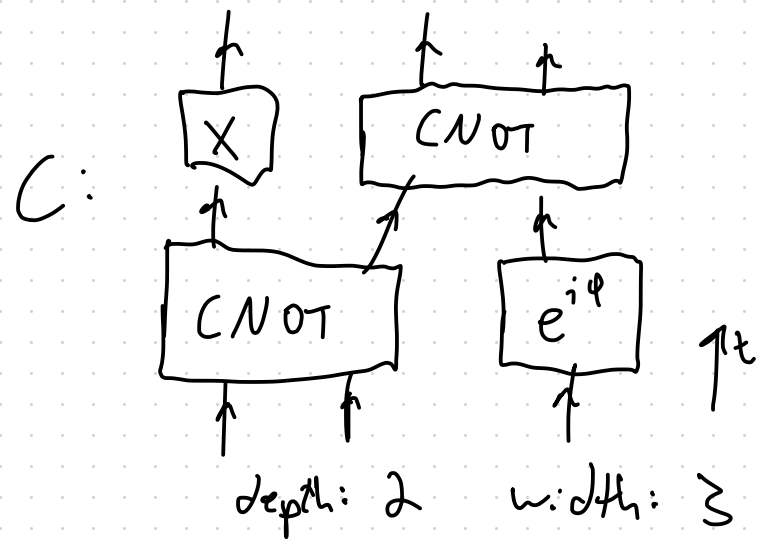
$$(X \otimes \text{CNOT}) \circ (\text{CNOT} \otimes e^{i\varphi})$$



Gate set \mathcal{G} is ^{precisely} universal if (for n large enough--)
every unitary $U: (\mathbb{C}^2)^{\otimes n} \rightarrow (\mathbb{C}^2)^{\otimes n}$ can be expressed
as a \mathcal{G} -circuit. (Every $U \in U(2^n)$ can be factored as
a product of elements of \mathcal{G} .)

$U(2) + \text{CNOT}$ is universal quantum gate set.

(in fact: phase gates + H + CNOT is universal.)

"Precisely universal" is overkill!

Why? Quantum computers are probabilistic and
states that are too close can not be feasibly
distinguished.

A better definition (but still arguably overkill...)

A gate \mathcal{G} is ^(player) quantum universal if for all n large enough, $\bar{\mathcal{G}}$ elements of \mathcal{G}^n in

$$U(\underbrace{\mathbb{C}^2 \otimes \dots \otimes \mathbb{C}^2}_n) \cong U(2^n)$$

(i.e., given $g \in \mathcal{G}$ that is binary, we get $n-1$ different unitaries of the form $I_{(\mathbb{C}^2)^{\otimes i}} \otimes g \otimes I_{(\mathbb{C}^2)^{\otimes n-2-i}}$)

generate (as a monoid) a dense subset

(For all $\epsilon > 0$ for every $U \in U(2^n)$, we can find a \mathcal{G} -circuit U' s.t. $\|U - U'\| < \epsilon$.)

Let

$$f: \{0,1\}^n \rightarrow \{0,1\}^m$$

be a function. A circuit U computes f to precision ϵ ($0 \leq \epsilon < 1/2$) if for any $x \in \{0,1\}^n$

$$\sum_{z=0}^{2^m-1} |\langle f(x), z | U | x, 0^{N-n} \rangle| \geq 1 - \epsilon.$$

\downarrow
0...0

(U has width N)