

Electric Circuit

- $i(t)$: current Amperes (A) $i(t) = \frac{dq}{dt}$
 $q(t)$: flow of charge coulombs (C)
 R : Resistance of a resistor ohm (Ω)
 C : capacitance of a capacitor Farads (F)
 L : inductance of an inductor Henrys (H)
- } constants.
- $E(t)$: Voltage gain of the current passing through the voltage source

Kirchhoff's 2nd Law: The sum of voltage drops around a closed circuit = 0

Voltage Drop $\Delta V_R = IR$

$$\Delta V_C = \frac{1}{C}q$$

$$\Delta V_L = L \frac{di}{dt}$$

$$0 = \Delta V_R + \Delta V_C + \Delta V_L - E(t) \Rightarrow L \frac{di}{dt} + Ri + \frac{q}{C} = E(t)$$

RC - circuit

$$i + \frac{1}{RC}q = \frac{E}{R} \Rightarrow \frac{dq}{dt} + \frac{1}{RC}q = \frac{E}{R}$$

1st order linear DE. $I(t) = e^{-\int \frac{1}{RC} dt} = e^{-\frac{t}{RC}}$

$$(e^{\frac{t}{RC}} q)' = \frac{E}{R} e^{\frac{t}{RC}} \Rightarrow e^{\frac{t}{RC}} q = EC e^{\frac{t}{RC}} + D \leftarrow \text{unknown}$$

$$q = EC + D e^{-\frac{t}{RC}}$$